
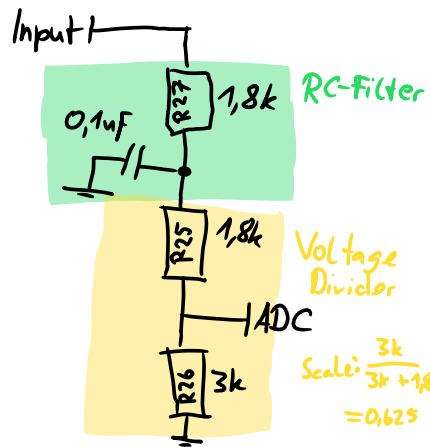



Circuit (for current sense)

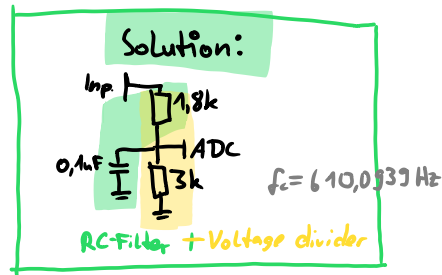


ISSUE:
Won't R27 & R25 form a 3.6k resistor and change the Voltage Divider scaling?



Equivalent Circuit

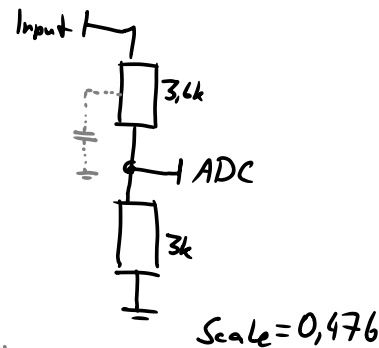

Circuit (for voltages)

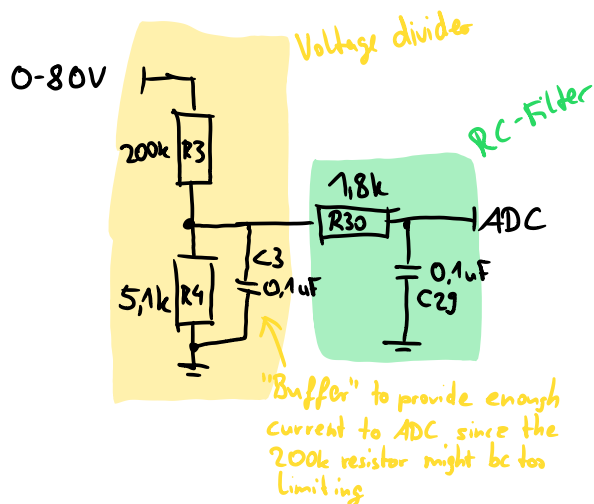


ISSUE:
Doesn't C3 form another RC-Filter with R3?

SOLUTION
Just remove C3

ISSUE 2:
R3 & R4 change the RC-filters corner frequency

new Circuit

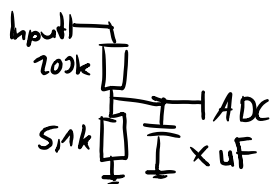

$$f_c = \frac{1}{2\pi(R_1 \parallel R_2)C}$$

$R_1 \parallel R_2$ = if R_1 & R_2 were parallel

$$\frac{1}{f_c} = 2\pi(R_1 \parallel R_2)C$$

$$C = \frac{1}{2\pi(R_1 \parallel R_2)f_c}$$

$$C = \frac{R_1 + R_2}{2\pi \times f \times R_1 \times R_2}$$

$$C(500\text{Hz}) = 6.4 \times 10^{-8} \text{ F}$$

$$C(500\text{Hz}) = 6.25 \times 10^{-7} \text{ F}$$

$$[f_c = 2\text{kHz}, 1\text{kHz}, 0.5\text{kHz}]$$

$$[f = 500\text{Hz}, R_1 = 20\text{k}, R_2 = 510\text{k}]$$

those are abit too small
for 80V (0.3W power loss)

$$f = 320,026 \text{ Hz}$$

$$[R_1 = 200\text{k}, R_2 = 5.1\text{k}, C = 0.1\text{uF}]$$